

How to Make a Thermal Flashlight:


1. Purchase the component parts:

Parts list

For a Thermal Flashlight with 5 V Melexis Sensor and Common Cathode LED.

- 1 [Melexis MLX90614](#) non-contact IR thermometer (5v).
- Data sheet: <http://www1.futureelectronics.com/doc/MELEXIS/MLX90614ESF-AAA.pdf>
- 1 [common-anode RGB LED](#)
- 2 4.7k Ohm resistors
- 2 100 Ohm resistors
- 1 180 Ohm resistor
- 1 0.1 μ F capacitor
- wire
- [a breadboard](#) or circuit board & soldering eqmt.
- [Arduino](#)
- 9v battery and holder
- Wire
- Wire Cutters

2. Build the Circuit Board

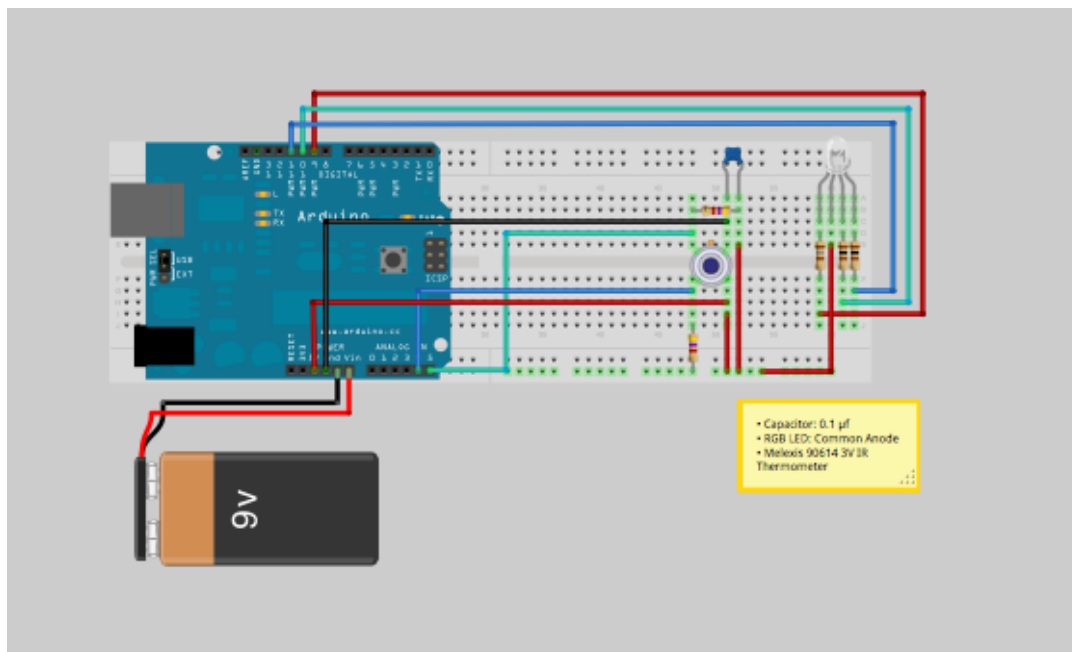


2.1 Place the Major components on the breadboard:

The circuit you are building connects temperature readings from the thermometer to different colors of light emitted by the LED through a Breadboard. You will learn later how to set both the range of the temperature and the colors of light emitted by the LED.

What are the Major Components?:

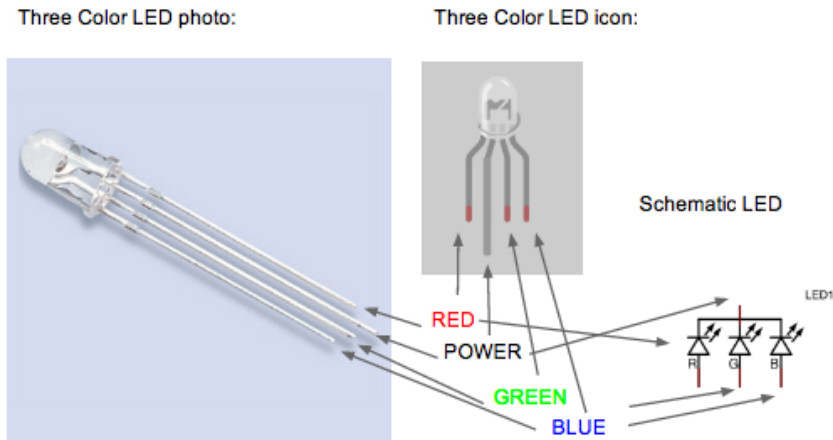Three color LED (light emitting diode) the three colors made by the LED red, blue and green will be blended to match different temperatures.




The Melexis non-contact thermometer. This thermometer senses the temperature of objects it is pointed at. The orientation of the thermometer is determined by the tab which should be pointed toward 12 o'clock.

Melexis 5V sensor




Photograph

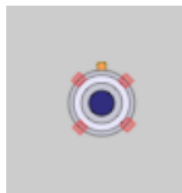


Icon

Schematic

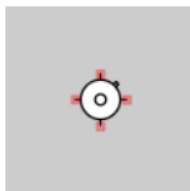


What is a Breadboard?:

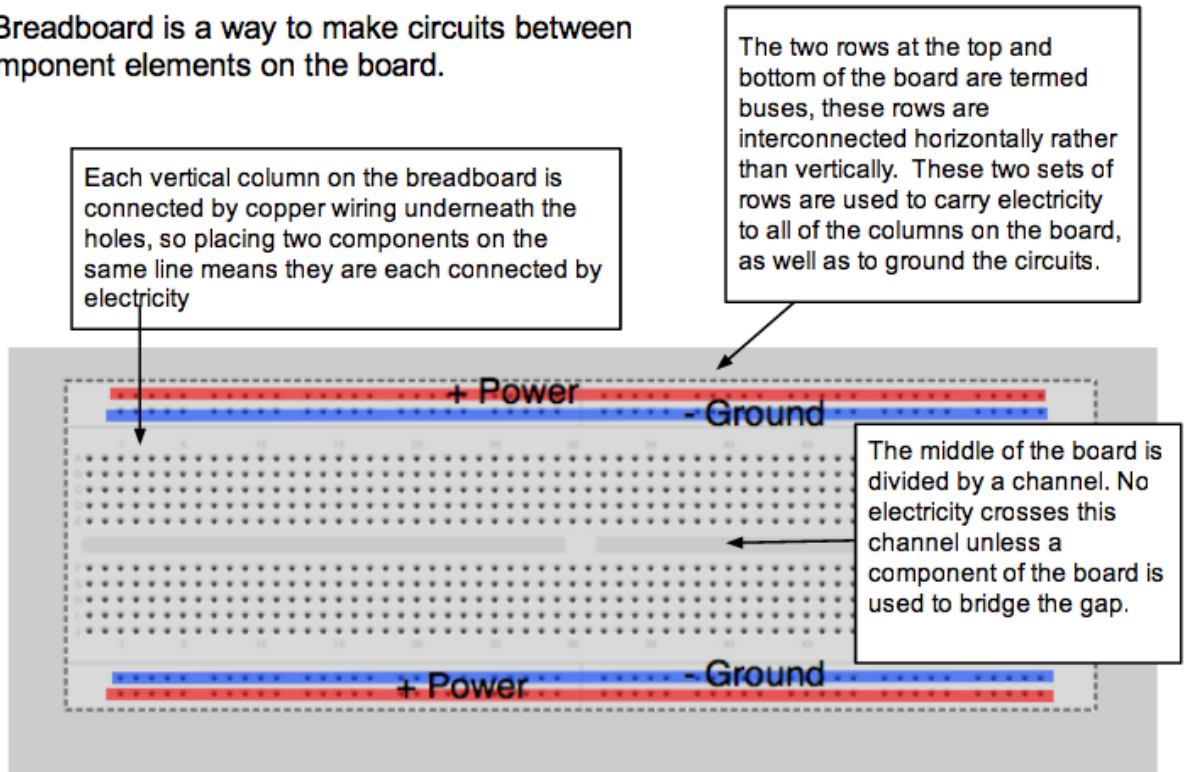A Breadboard is a way to make circuits between component elements on the board.



Where should I place them on the Breadboard?

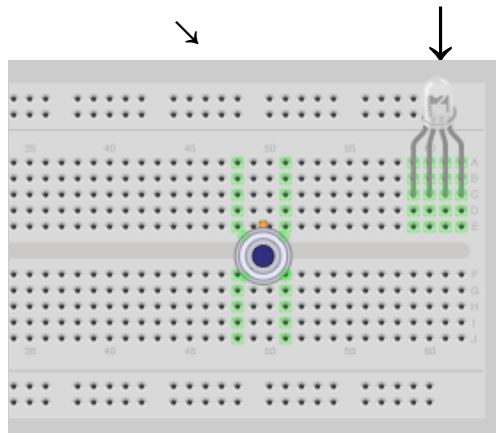Close together! The flashlight should change color based on what the temperature of the object the sensor points at. So that the light shines on the object whose temperature you are interested in sensing, you should place the LED and Sensor close to each other on the breadboard.




1. Each "leg" of the LED and the sensor should go in one hole of the breadboard.
2. Orient the LED so the long leg (power) is in the second position from Left to Right
3. The Nub on the sensor should face to 12 o'clock, this sets the directionality of the legs.

2.2 Create a Circuit between the Components:


The next step is to create a circuit between the LED and Sensor using common electronic components: Resistor and Capacitors. The LED and the Sensor require different quantities and electricity, the amount of electricity to each component is managed using resistors and capacitors.

2.3 Select your resistors and capacitor.

Sensor Resistors: two 4.7 k Ω

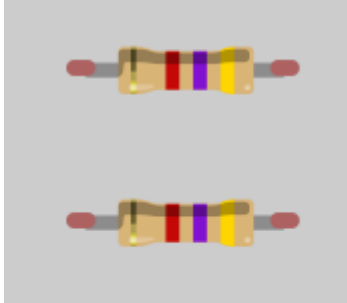


Sensor Capacitor: one 0.1 μ F capacitor

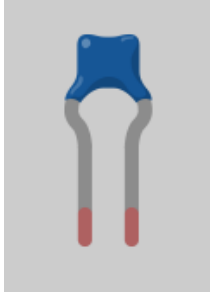


LED Resistors: one 180 Ω resistor




and two 100 Ω resistors

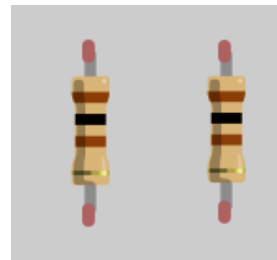

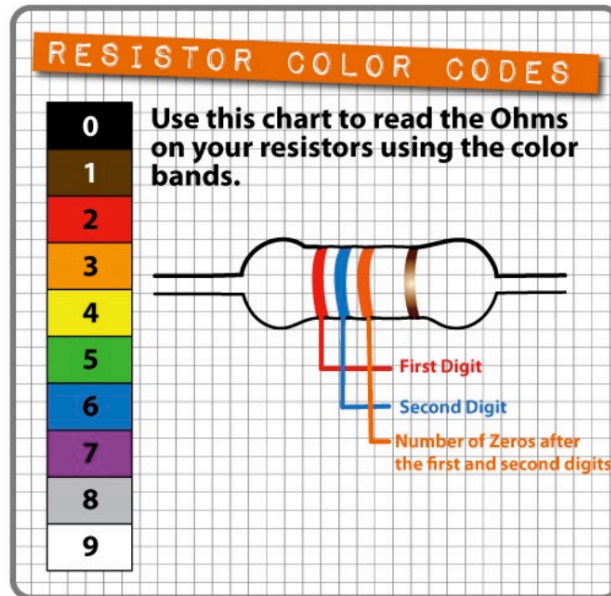

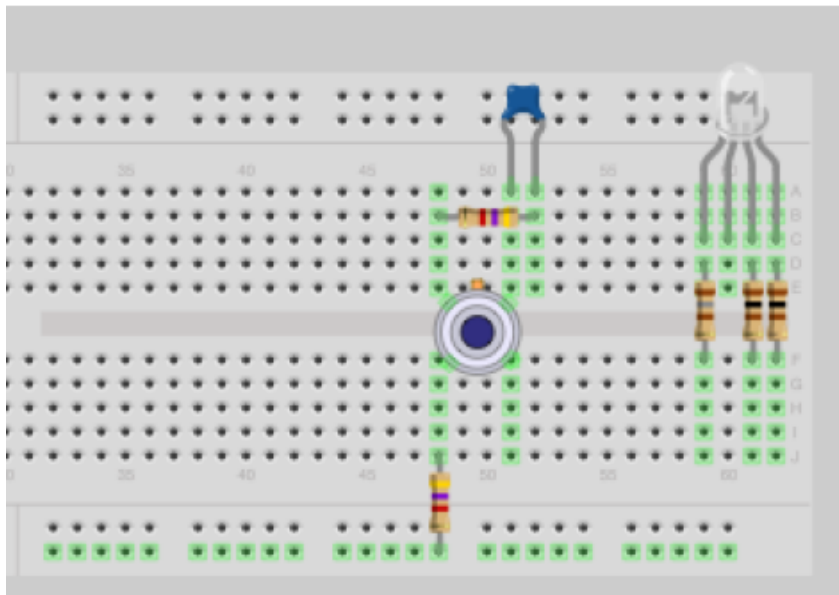2.4 Put your resistors and capacitor into the breadboard


Trim the legs of the resistors with wire cutters and place them in the breadboard according to this diagram:



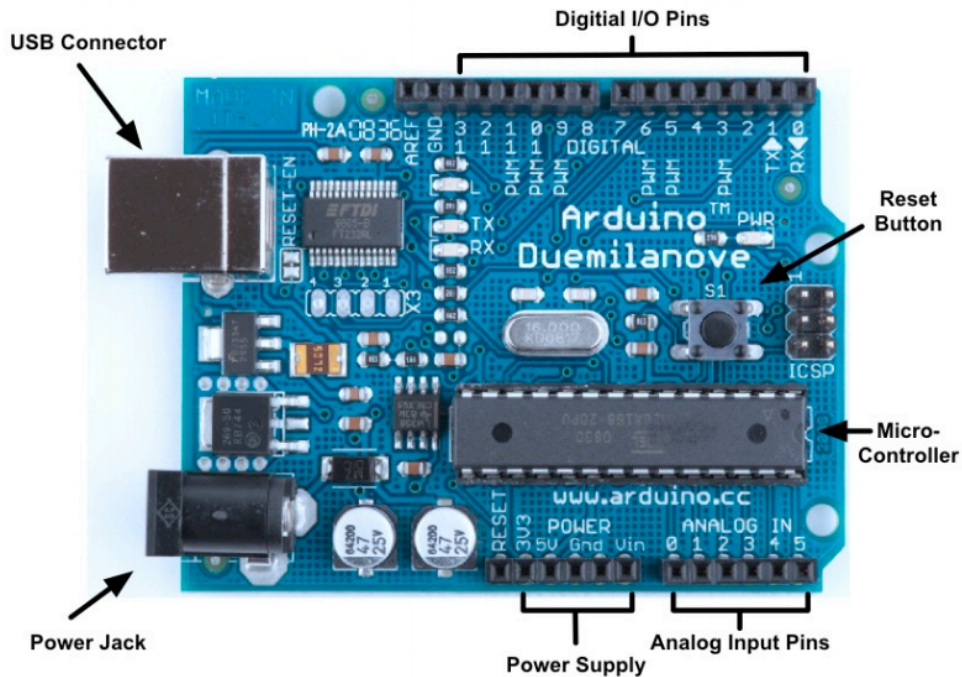2.5 Grab your Arduino!

What is an Arduino?

- * A Microcontroller you can program
- * Inputs and outputs
- * Memory



- **open-source hardware and software** prototyping platform
- will allow us to **control** the flow of electricity **and** let us **measure** electricity through **CODE**

```

ThermalFlashlight
// See http://bitdr.org/2011/02/mlx90614-arduino/ for i2c library and instructio
// You must download the "twimaster.cpp" and "i2cmaster.h" files, and place them
// Typically, once you install these files, you must relaunch Arduino.

// The extra files are included in this Gist, as well as attached to the page ht

#include <i2cmaster.h>
#include "Wire.h"
#include "BlinkM_funcs.h"

const float lowReading = 65;
const float highReading = 90;
const unsigned char separatorCharacter = 255;


void setup(){
  pinMode(9,OUTPUT);
  pinMode(10,OUTPUT);
  pinMode(11,OUTPUT);
  Serial.begin(9600);
  Serial.println("starting setup...");

  i2c_init(); //Initialise the i2c bus
  PORTC = (1 << PORTC4) | (1 << PORTC5); //enable pullups
  Serial.println("completed setup");
}


```

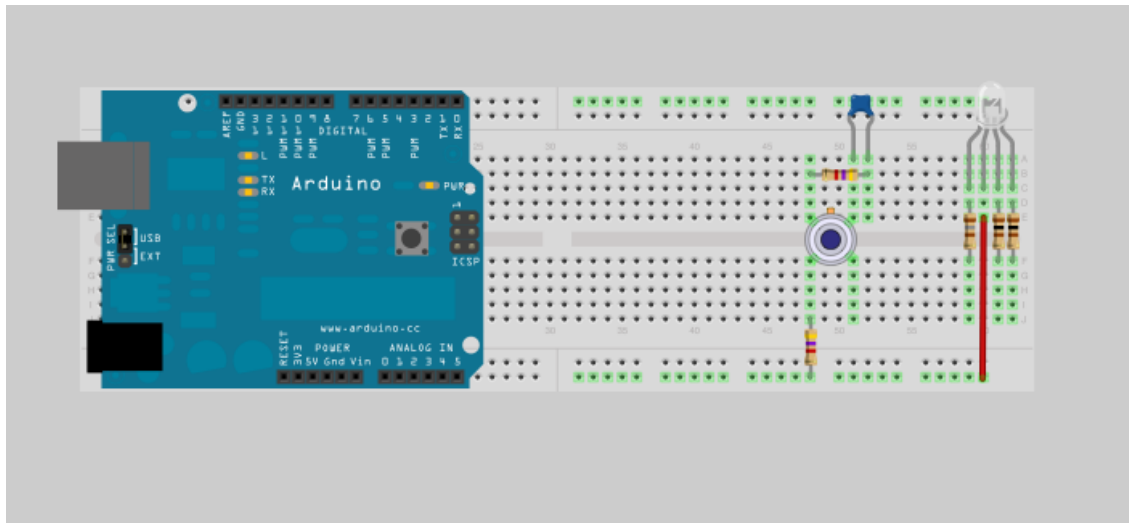2.6 Wiring LED to Arduino

Step 1: Take power to the LED.
Which leg should it go to?



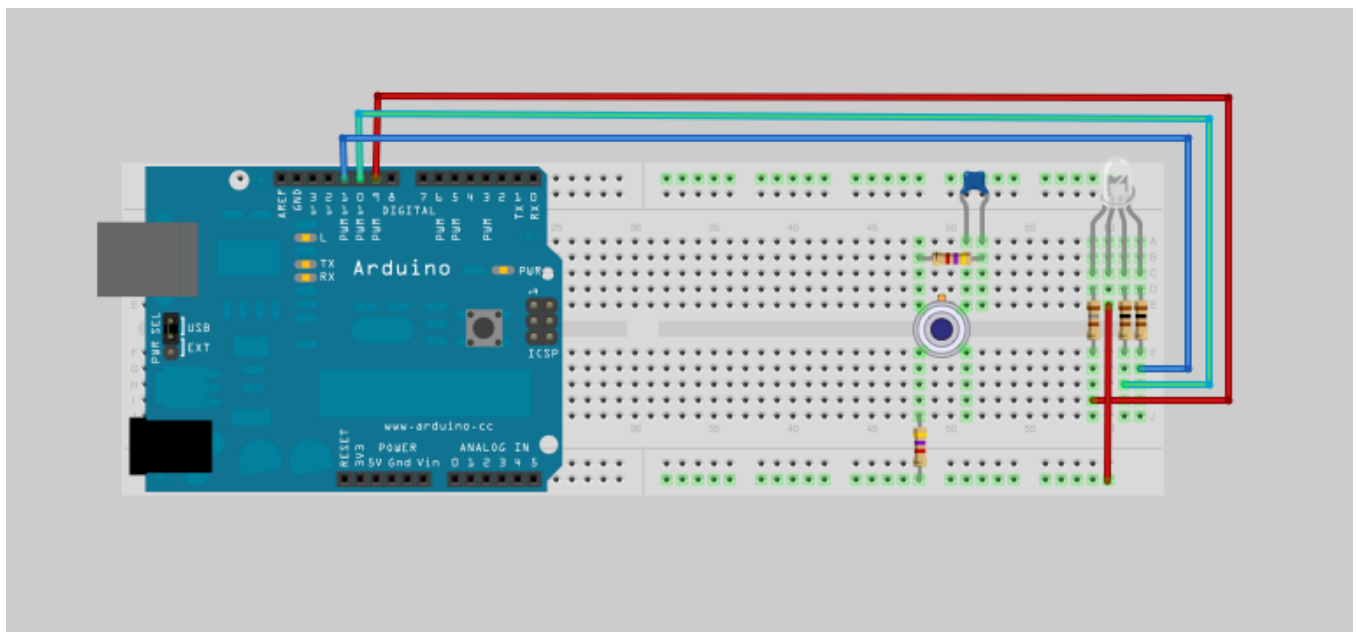Step 2: Connect up the RED, GREEN and BLUE legs of the LED to Digital pins 9, 10 and 11



DONE!

2.7 Wiring the Sensor to the Arduino


Step 1:

Bring Power to the Sensor!

The sensor has a little computer inside it so it needs power to two points.

Connect one wire to the capacitor. Make sure to jump the gap!

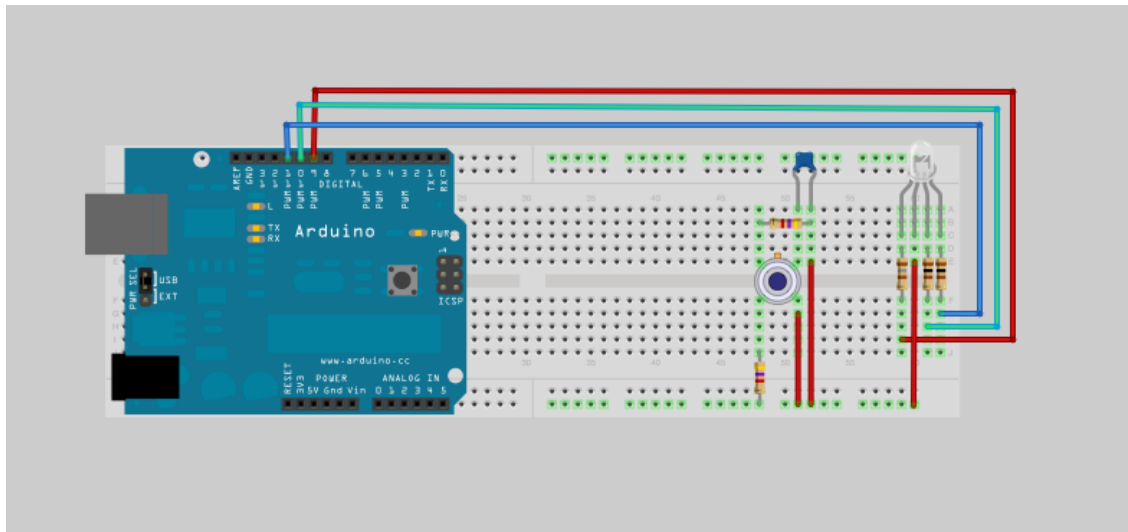
Connect one wire to the bottom right leg of the sensor.



Step 2:


Bring Power to the Board!

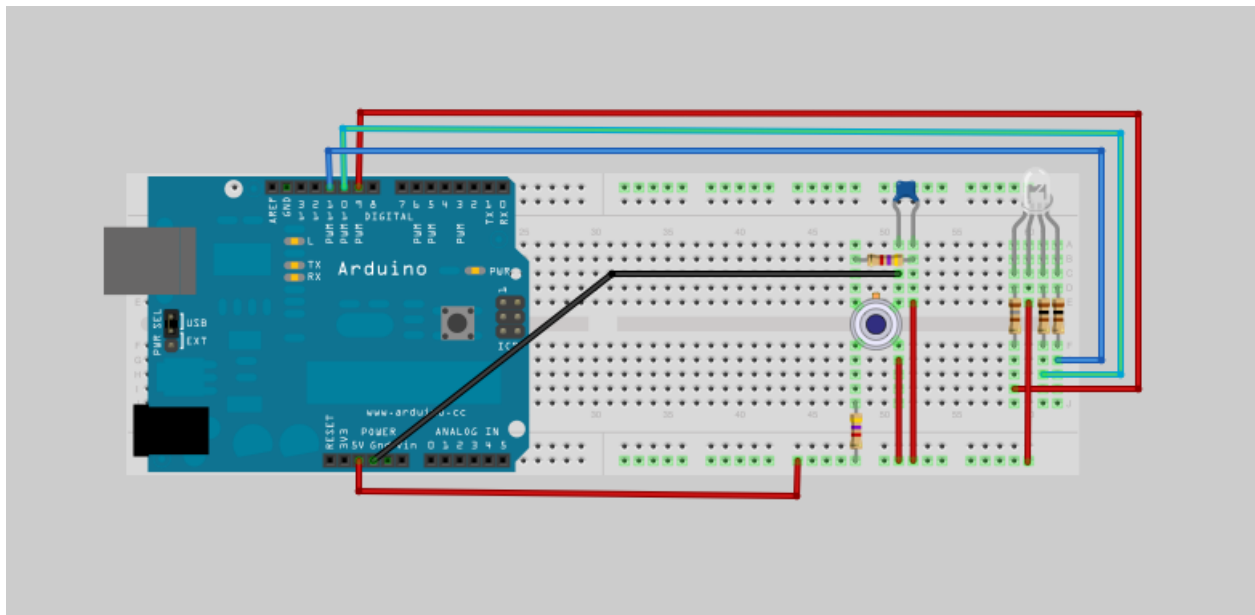Connect the 5V pin on the Arduino to the Power bus on the board
And connect the top right leg of the capacitor to the Ground (GND) pin.



Step 3: Bring Data to and from the Sensor

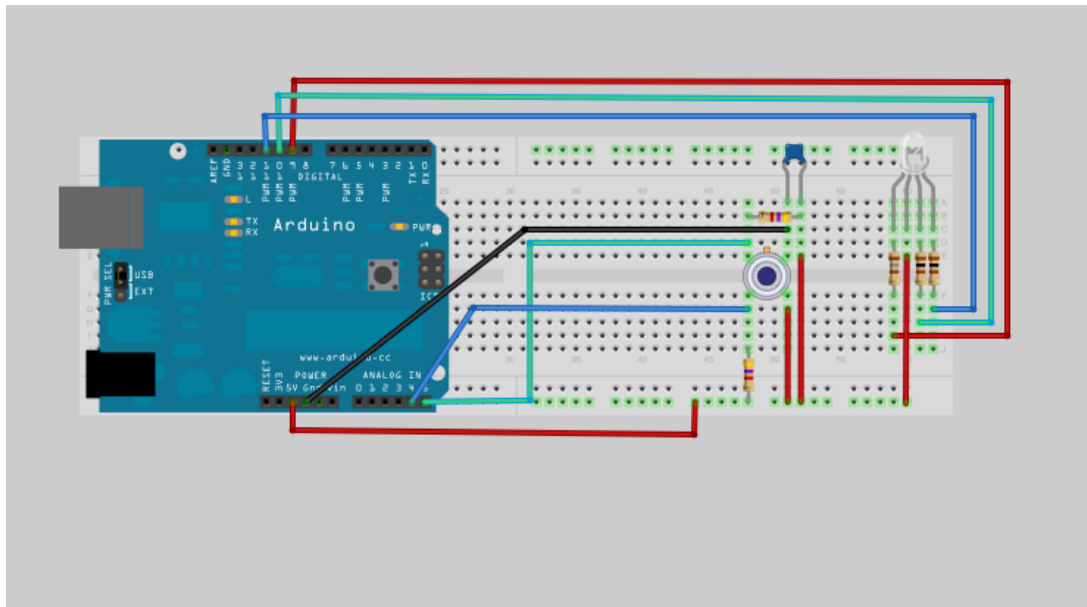Connect one wire from the top left leg of the sensor to ANALOG pin 5.
Connect one wire from the bottom left leg of the sensor to ANALOG pin 4



2.8 FINAL STEP!

Plug in the board--Use either a battery, or plug into a computer

Connect Black wire to Ground (GRN)

Connect Red wire to Voltage in (VIN)

The LED should light up

